

Project

VLSI for Digital signal processing

Topic: 9 tap FIR filter implementation

Presented by:

Jyotika Kumari (20224077)

Sakshi Singh (20224128)

Shivani (20224144)

Shrestha Katiyar (20224149)

Tushita Katiyar (20224166)



What is a Filter???

A filter is a device or process that removes unwanted components or features from a signal.

Application:

1. Audio processing (removing noise)
2. Image processing (smoothing or sharpening)
3. Communication systems (selecting signal bands)

what is FIR filters???

A Finite Impulse Response (FIR) filter has a finite duration response to an impulse input.

An FIR filter of order N is defined by the difference equation:

$$y[n] = b_0x[n] + b_1x[n-1] + b_2x[n-2] + \dots + b_Nx[n-N]$$



Impulse Response:

The impulse response of an FIR filter is just its coefficients:

$$h[n] = \{b_0, b_1, \dots, b_N\}$$

Properties of FIR

  1. Linear Phase:
2. Always Stable:
3. Simple Implementation
4. No IIR Feedback



9 tap FIR filter

We have made a 9 tap FIR filter with the following specifications and using 6 stage pipelined structure:

Input frequency (f_c) : 10 MHz

Sampling frequency (f_s) : 100 MHz

$f_1=2\text{MHz}$, $f_2=30\text{MHz}$

Coeff 0 = 57.	coeff4 = 8879	coeff 8=166
---------------	---------------	-------------


Coeff1 =166.	coeff 5 =7187
--------------	---------------

Coeff2 = 962.	coeff 6=3629
---------------	--------------


Coeff3 = 3629.	coeff 7=962
----------------	-------------


Non pipelined design

•

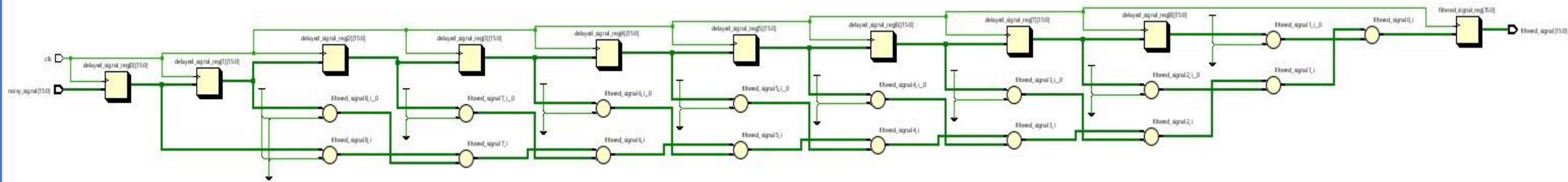

Pipelined design

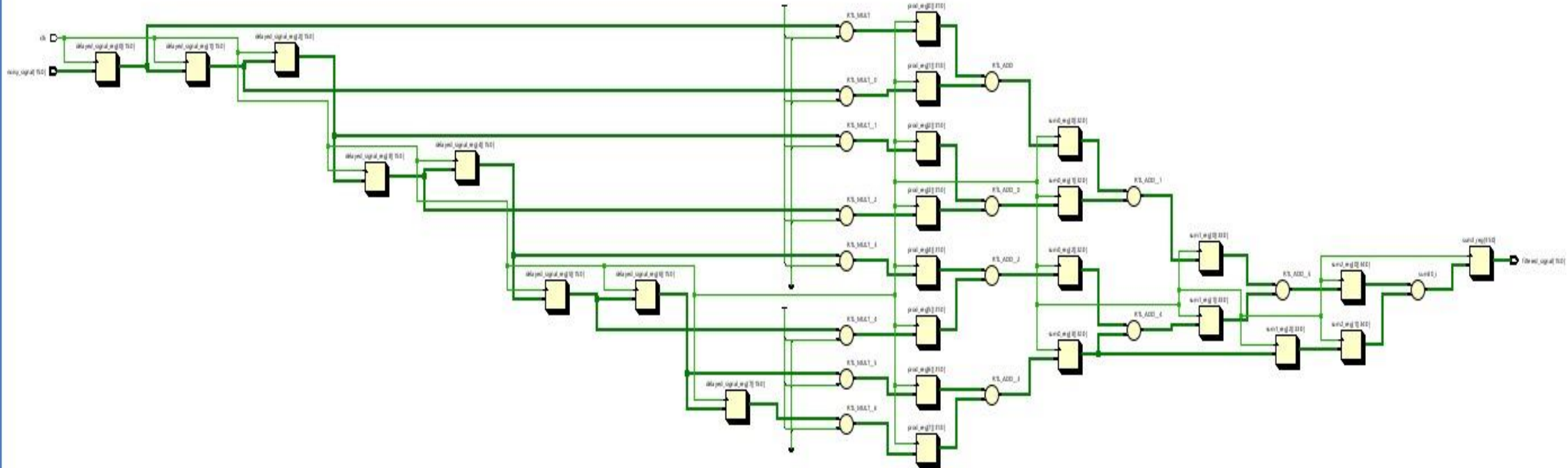

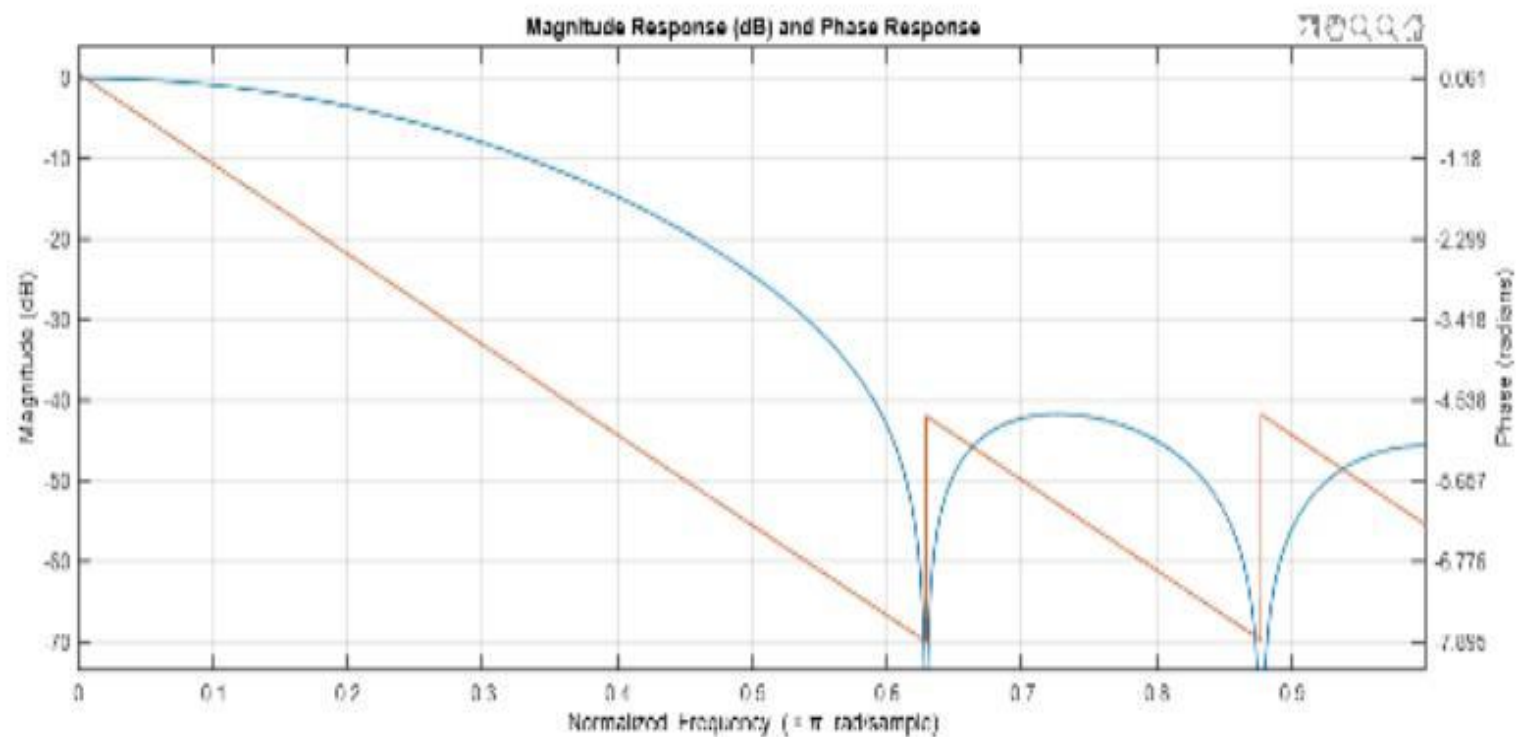

magnitude and phase response


Name	Slack ^{^1}	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock	D
Path 1	∞	8	1	filtered_signal1/CLK	filtered_signal0_6/PCIN[0]	13.728	13.728	0.000	∞		
Path 2	∞	8	1	filtered_signal1/CLK	filtered_signal0_6/PCIN[10]	13.728	13.728	0.000	∞		
Path 3	∞	8	1	filtered_signal1/CLK	filtered_signal0_6/PCIN[11]	13.728	13.728	0.000	∞		
Path 4	∞	8	1	filtered_signal1/CLK	filtered_signal0_6/PCIN[12]	13.728	13.728	0.000	∞		
Path 5	∞	8	1	filtered_signal1/CLK	filtered_signal0_6/PCIN[13]	13.728	13.728	0.000	∞		
Path 6	∞	8	1	filtered_signal1/CLK	filtered_signal0_6/PCIN[14]	13.728	13.728	0.000	∞		
Path 7	∞	8	1	filtered_signal1/CLK	filtered_signal0_6/PCIN[15]	13.728	13.728	0.000	∞		

timing analysis of non pipelined


Name	Slack ^{^1}	Levels	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement
Path 1	∞	2	1	sum3_reg[15]/C	filtered_signal[0]	5.441	3.055	2.385	∞
Path 2	∞	2	1	sum3_reg[19]/C	filtered_signal[4]	5.430	3.063	2.367	∞
Path 3	∞	2	1	sum3_reg[17]/C	filtered_signal[2]	5.429	3.053	2.376	∞
Path 4	∞	2	1	sum3_reg[16]/C	filtered_signal[1]	5.423	3.050	2.373	∞
Path 5	∞	2	1	sum3_reg[18]/C	filtered_signal[3]	5.409	3.054	2.355	∞
Path 6	∞	2	1	sum3_reg[20]/C	filtered_signal[5]	5.381	3.054	2.327	∞
Path 7	∞	2	1	sum3_reg[23]/C	filtered_signal[8]	5.250	3.070	2.180	∞

timing analysis of pipelined


On-Chip Power

 


On-Chip Power

 

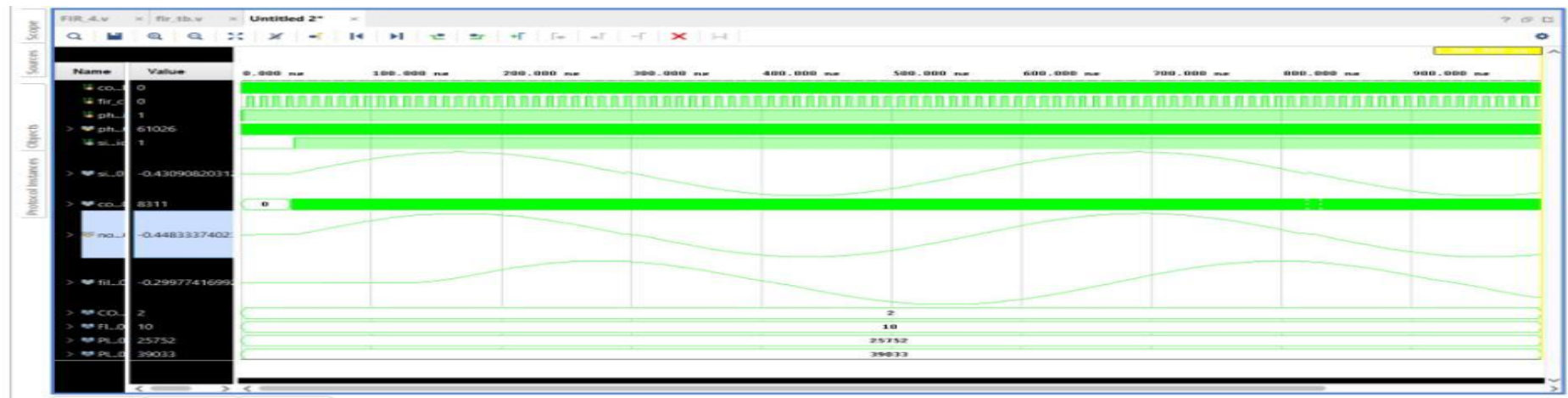
power analysis of pipelined (2) and non
pipelined (1)



output when input is $f_1 = 2\text{MHz}$

 

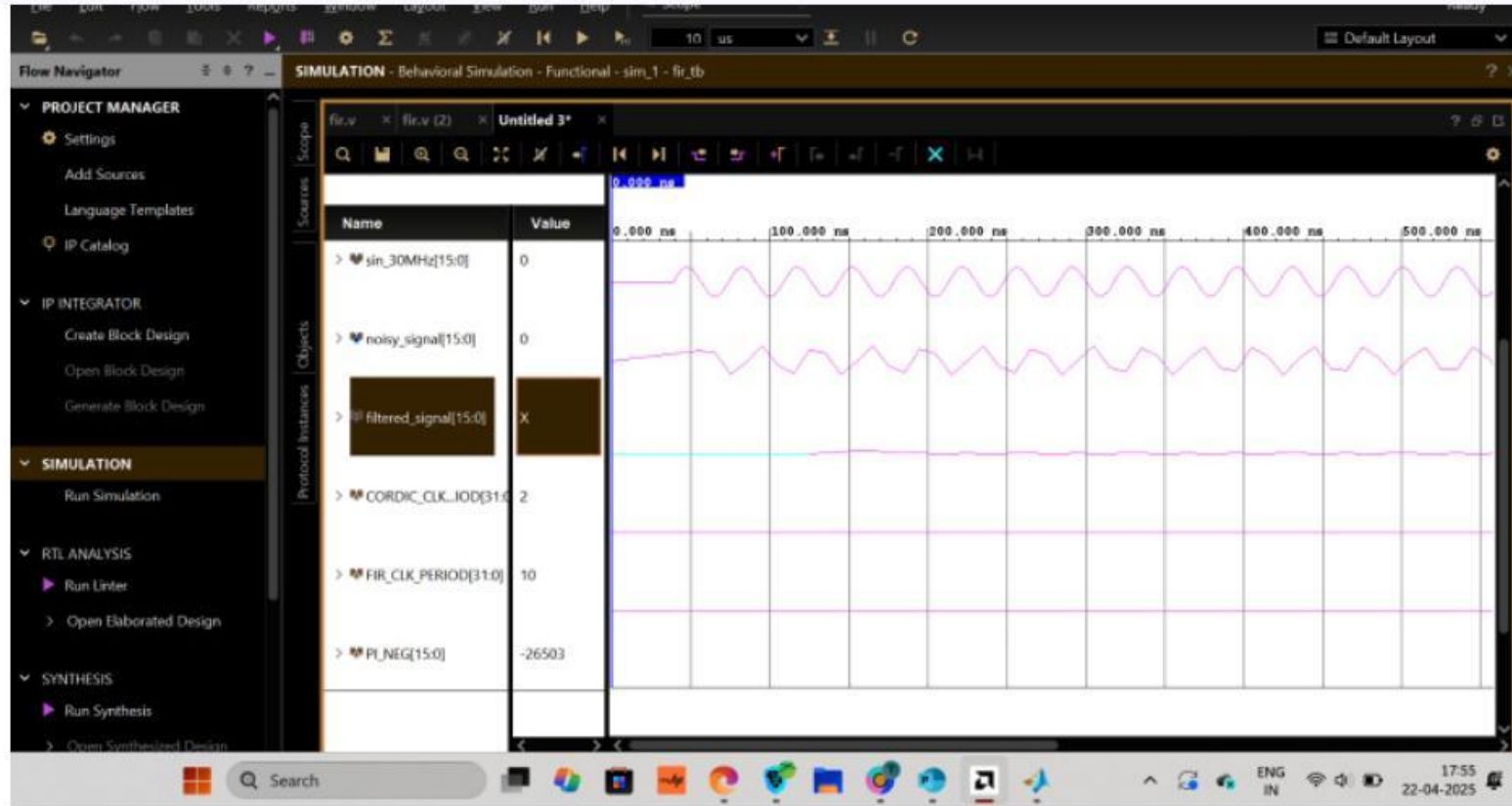output when $f_1 = 2\text{ MHz}$ and $f_2 = 30\text{ MHz}$ are given



output when $f_2 = 30\text{MHz}$ is given